


Presentation of Liaison

Voting system for extraterrestrial space craft


Presentation Outline

- What does our system do?
- How does it do it?
 - Block diagram
 - Algorithms
- System performance
 - Area
 - Timing


System Overview

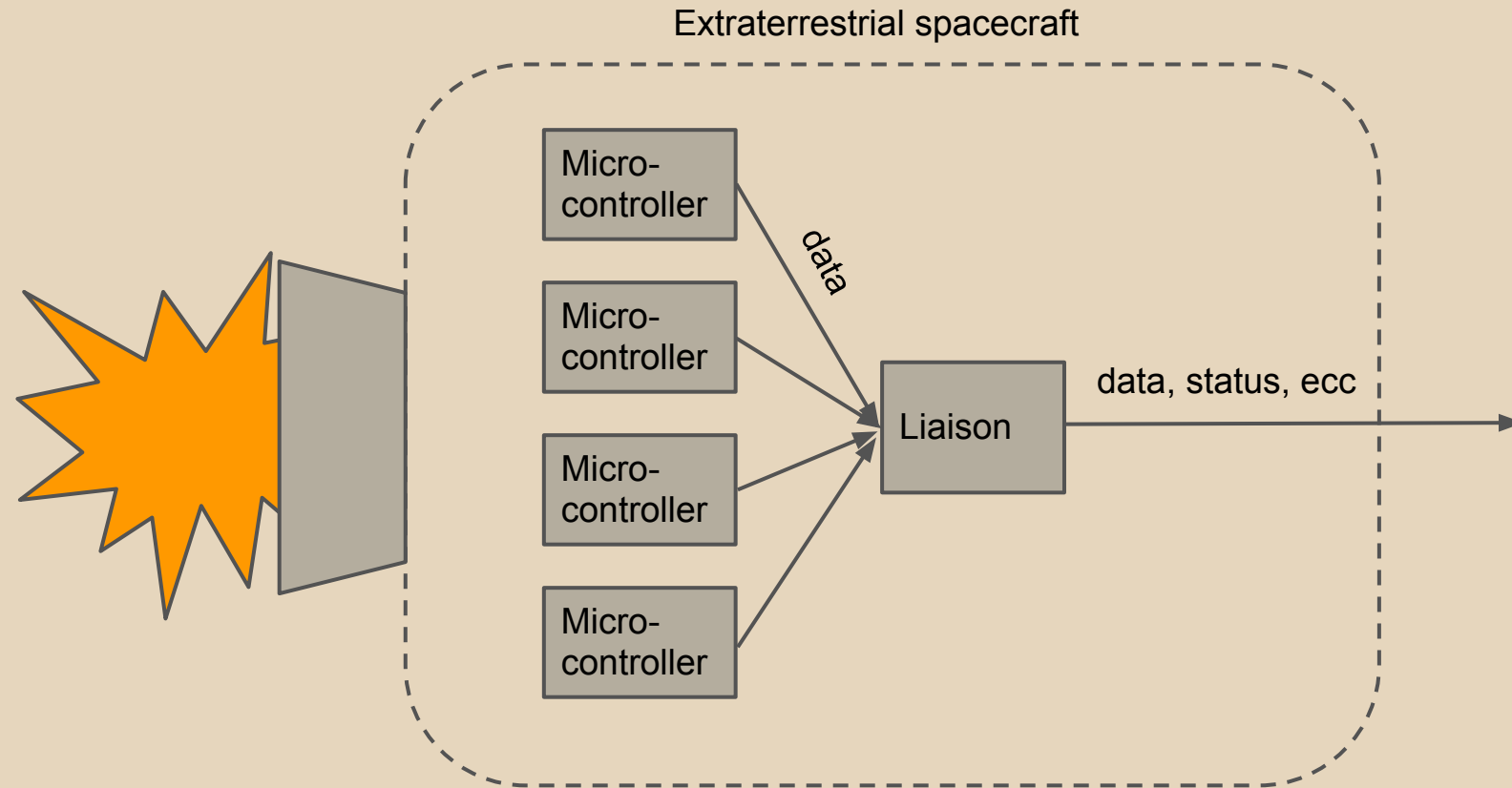


Block Diagram

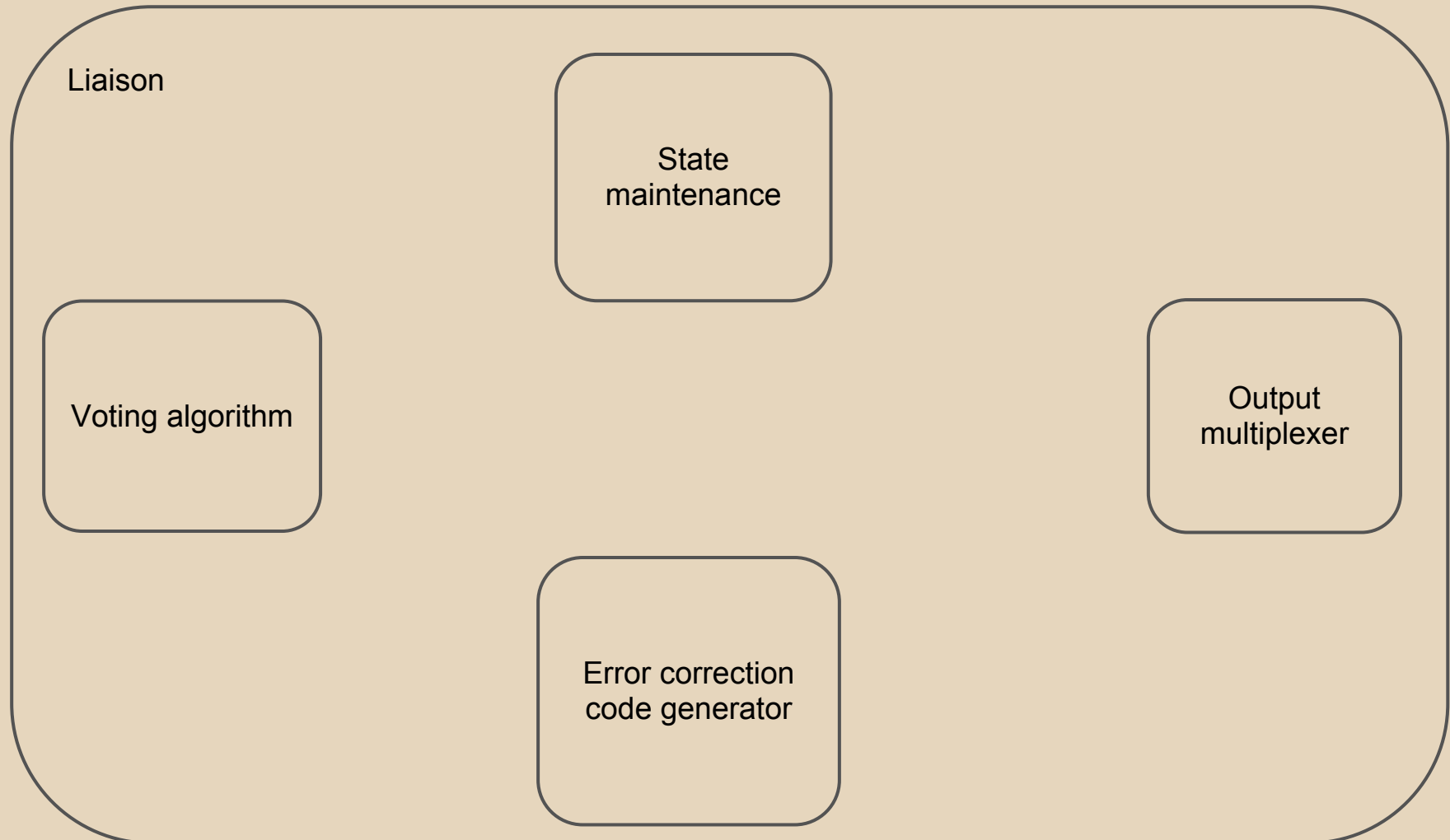


Block Diagram

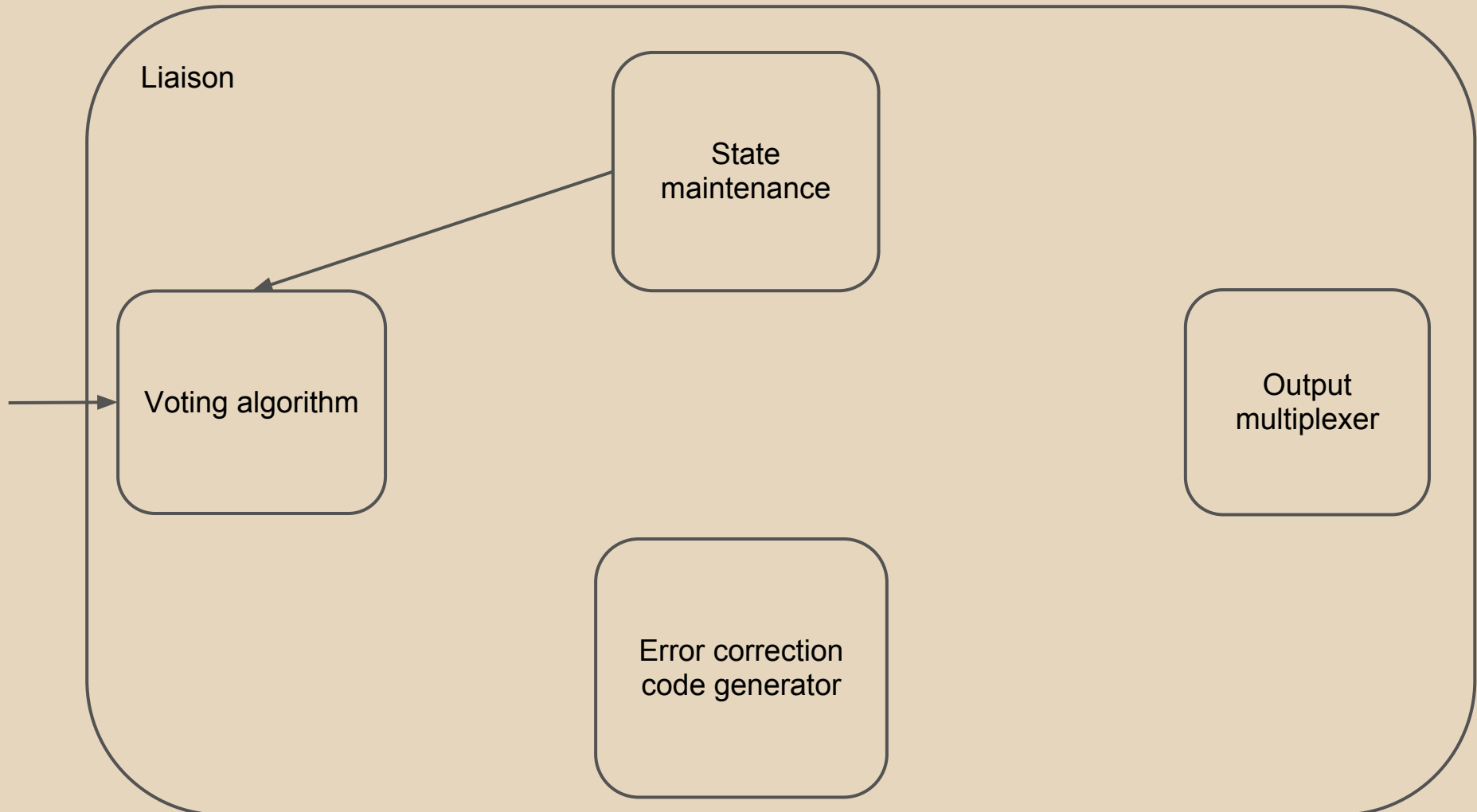


Block Diagram

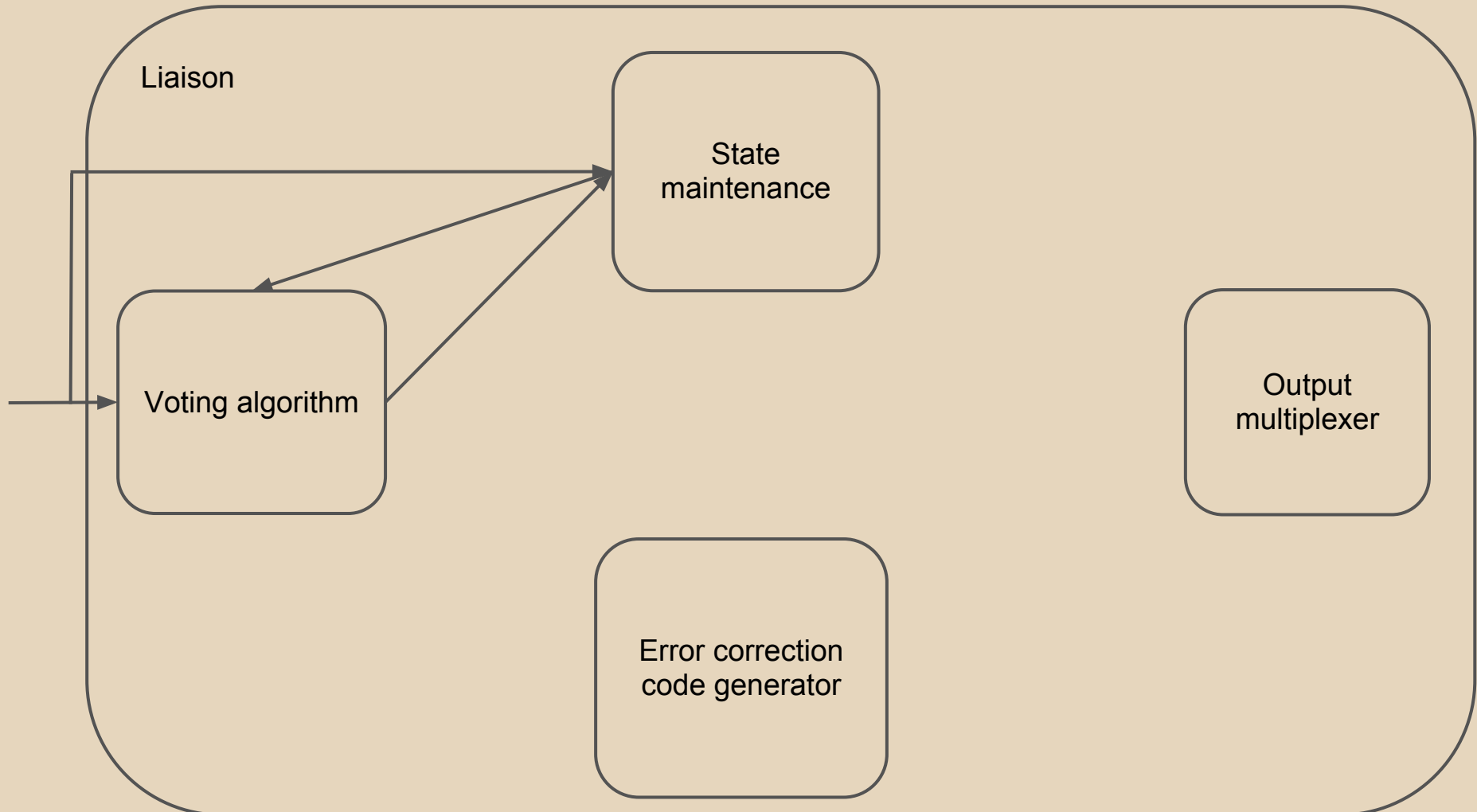

Block Diagram

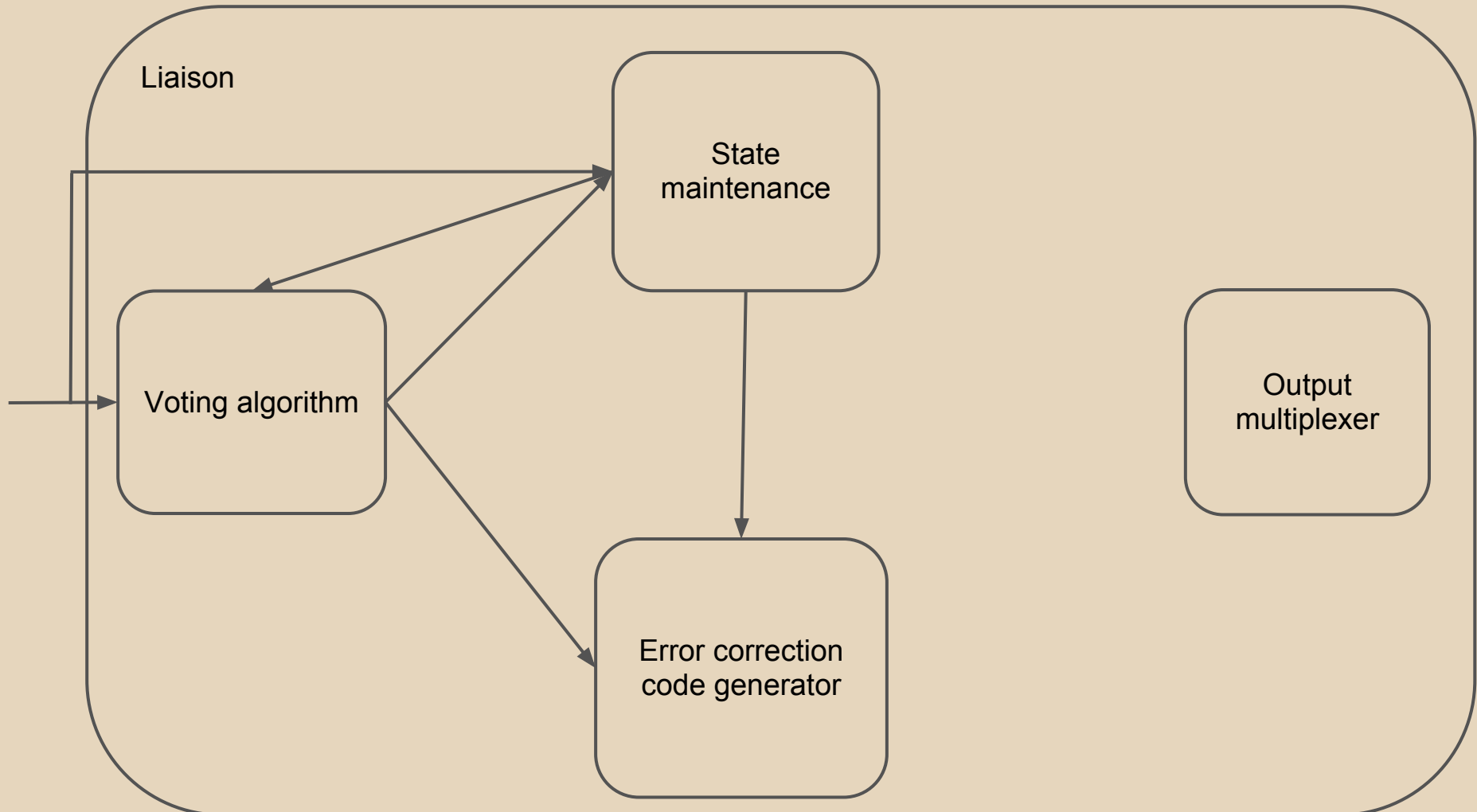

Block Diagram

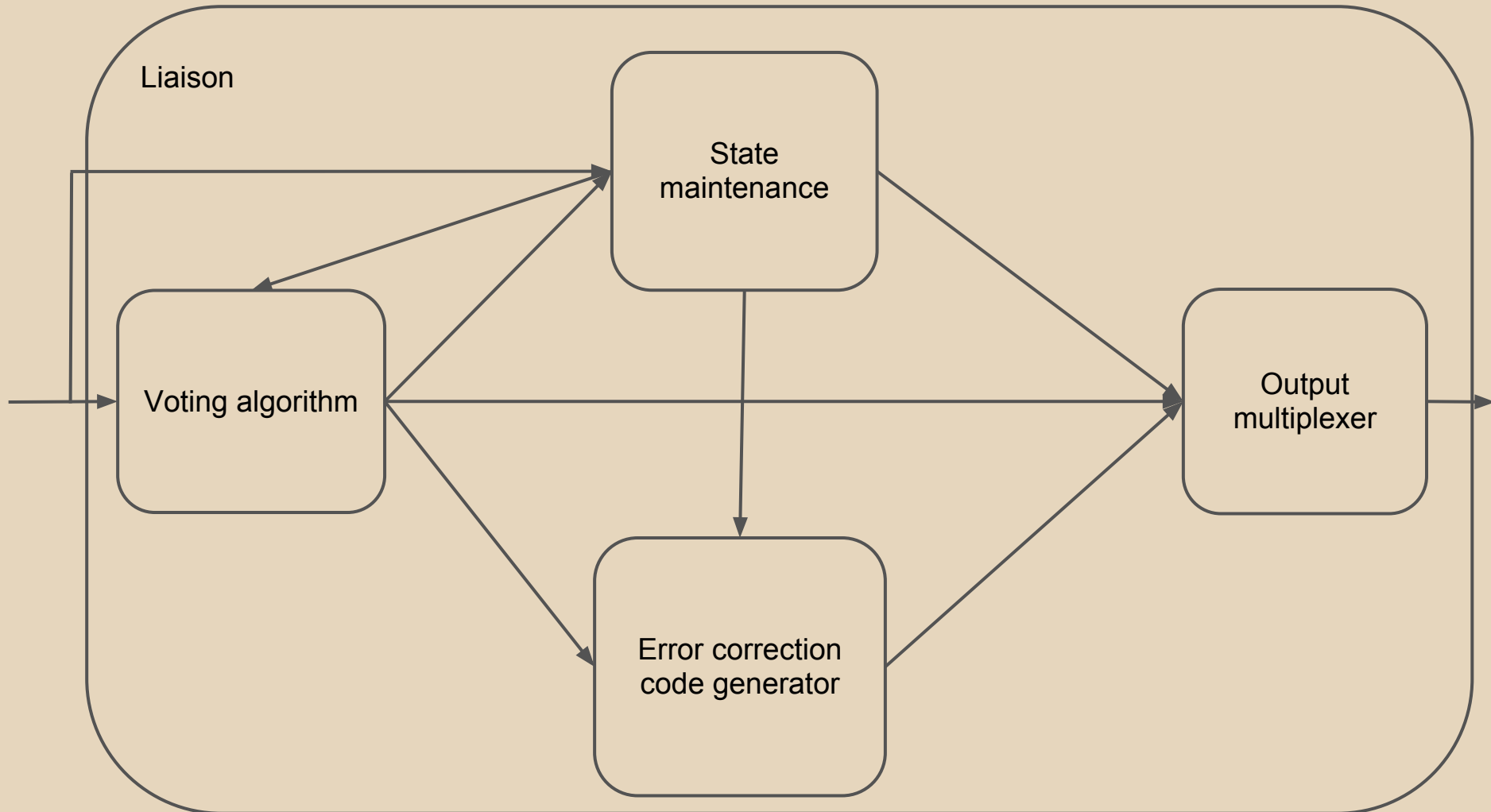

Voting Algorithm

- MCUs are designated by A,B,C and D, and they are tagged if the system detects a false value
- The MCUs are assigned in groups of (A,B) and (C,D)
- Each group have a "local vote", where the first is chosen if it works, else the second is chosen if it works, else '0' is voted.


Voting Algorithm

- If both A and B works and agree on output, it is always safe to select result from (A,B)
- Else if C and D agree, it is safe to select the result from (C,D)
 - (A,B) is not safe, thus counts as one vote.
 - (C,D) counts as 2,1 or 0 votes, according to state.
 - This means majority, decisive vote or broken
- Else if C and D does not agree, the answers from (A,B) and (C,D) are ORed together, since neither of the groups represent the majority

State Maintenance

- The internal state is represented by three state elements
 - Output stage
 - Error tags
 - Intermediate parity bits calculation
- The output stage is a one-hot 16-flip-flop shift register
- The error tags are set when a MCU gives different result than voted output
- The parity bits are calculated using current output combined with the output stage

Error Correction

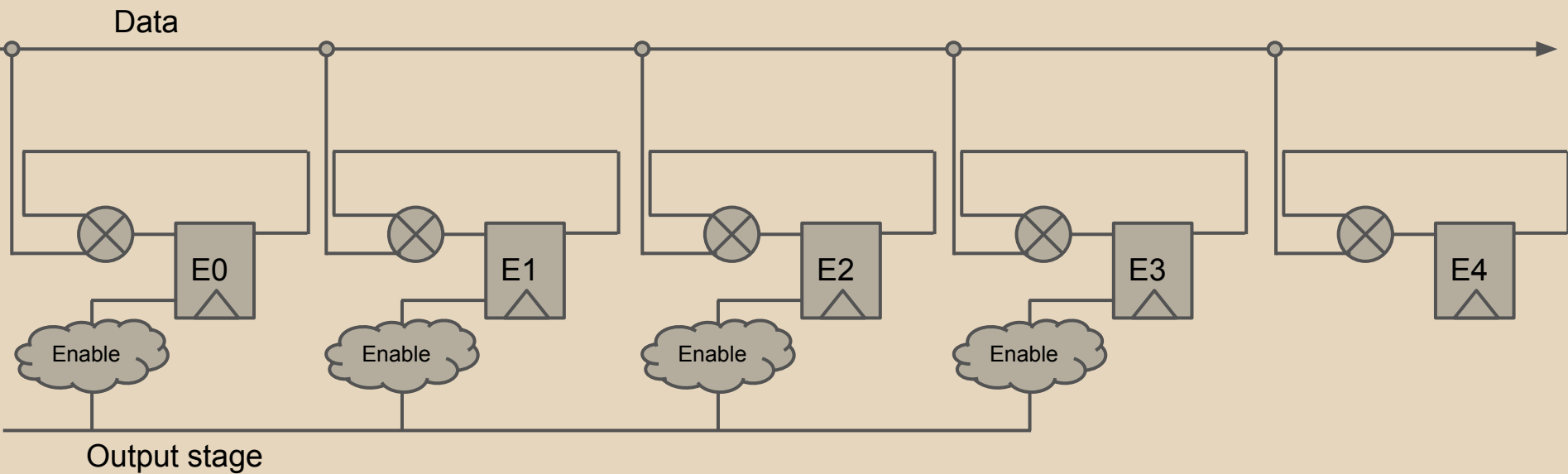

Output Multiplexer

- Selects what bit is sent
 - Voted data
 - System status
 - ECC
- Selected output is defined by current output stage
- When ECC bit 4 is sent, it is XORed with the other ECC-bits


Area

- The circuit is realizable with 32 LUTs
 - Xilinx XST - 32 LUTs with area optimization
 - Synplify Pro - 37 LUTs with disabled sequential opt.
- Voting: 6 LUTs
- State maintenance w/o ECC: 4 LUTs
- ECC: 11 LUTs
- Output Multiplexing: 8 LUTs
- Status calculation: 3 LUTs

Verification

- Test bench
 - 7 tests for ordinary flow
 - 24 distinct corner cases
 - 16836 tests for all permutations fail states
 - All permutations of fail states
 - All 256 possible inputs (all MCUs agree)
 - Assures that each input is correct for any state.
- Test-driven development
 - Wrote a lot of tests, improved design until both LUT count was minimal and all tests were good

Timing

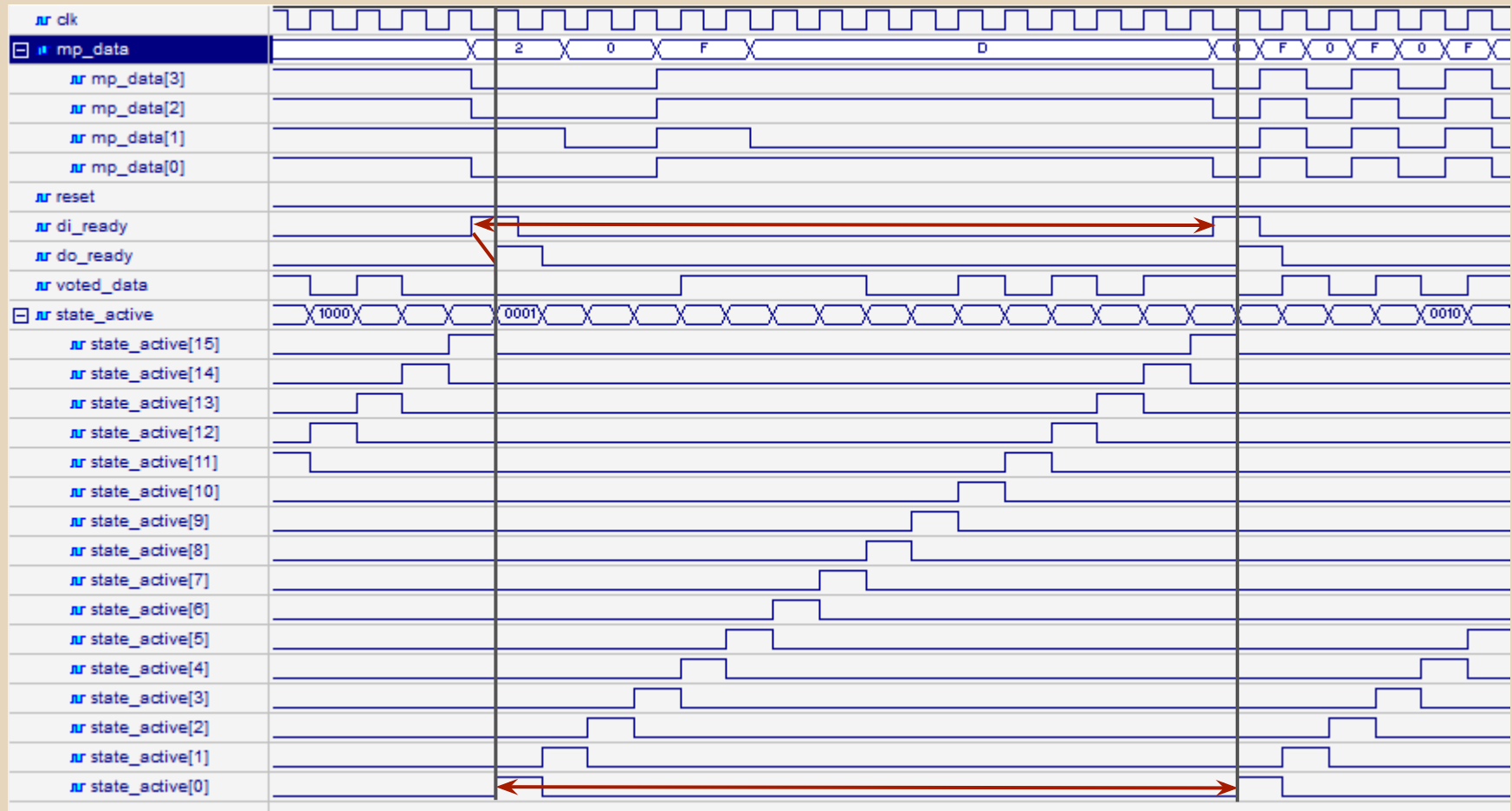

Questions?